

CHALLENGER IP VIDEO DISPLAY MODIFICATIONS

Copyright C. 1979 by Steven Chalfin

328 Queen Street

Phila., PA 19147

All Rights Reserved

INTRODUCTION:

The CHALLENGER IP (SUPERBOARD II) computer system is one of the best values in hobby computers today. Its many outstanding features are well known. However, its low price has necessitated several design compromises. One of these compromises involves the video display circuitry. The advertised 32x32 format is actually only 24x24 or at best 26x26 on a standard television. Even if a high quality monitor is used and the display size can be increased, the BASIC in ROM will still limit the line length to 24 characters.

Adding guard band circuitry would give a true 32x32 display on a standard television, but would be both expensive and technically difficult to implement. The most cost-effective solution this author has found, and the one which is described in this manual, is outlined below:

- 1) Double the dot clock frequency. This has the effect of putting out twice as many dots per scan line (twice as many characters per line).
- 2) Since there will be twice as many characters per line but the same number of lines on the screen, an additional 1K of video memory must be added.
- 3) Associated circuit changes for memory decoding, sync pulses, etc.
- 4) A software patch so that BASIC will use the entire screen to display.

These modifications yield a 32 line x 64 character display. Since this circuitry still lacks guard band capability, some characters are lost off the screen due to overscan. However, the resultant 30 line x 50 character display is a vast improvement.

It is assumed that the person undertaking this conversion is familiar with such basic electronic construction techniques as soldering and reading schematics. Components required for this conversion are:

QUAN	DESCRIPTION
4	2114 or 2114L 450nS or faster RAM*
1	8.0 MHz crystal
1	74LS163 or 74LS161 4 bit binary counter+
1	74LS139 2 to 4 decoder (dual)+
2	16 pin DIP sockets

*This is critical! Don't buy slower (cheaper) RAMs as they will not work.

+Be sure to use the 74LS series, not the 74 series as these are slower and may not work.

Also required: Model 600 schematic, solder, #30 AWG wire wrap wire, soldering iron, wire stripper, razor blade or X-acto knife.

These parts may be had for \$40 or less, depending on how well stocked your junk box is.

STARTING ON THE RIGHT FOOT:

Unless you have absolute confidence in the quality control procedures of IC manufacturers you should test the parts which will be used in this conversion. The easiest way to do this is simply to substitute them for equivalent parts on the 600 board.

First, remove the six screws securing the bottom of the case. Then remove the six screws securing the 600 board to the top of the case. Carefully unplug the power and interface connectors and place the board on a clean work surface, component side up. Carefully remove U57 and replace it with your new 74LS163. Carefully remove U17 and replace it with your new 74LS139.

Carefully remove the video RAMs (U39, U40), which will not be used in the new circuitry, and replace with 2 of the new 2114's. Recheck the orientation of the new chips. Reconnect the 600 board. Turn on the power. Try reading programs by cassette, printing on the screen, etc. to make sure everything is working. Run a memory test program on the video RAM space 53248-54272 decimal or D000 to D3FF hex. A short, but slow program is shown below:

```
10 FOR I=53248TO54272:FOR J=0TO255
20 POKEI,J:IF PEEK(I)<>JTHENSTOP
30 NEXT:NEXTI
40 ?"OK"
```

BREAK IN 20 indicates a memory read or write error. If everything looks good remove the board again and replace the two new video RAMs with the two remaining new 2114's. Reinstall the board and rerun the memory test program. If everything checks out remove the board once again.

SPEEDING UP THE CLOCK:

Unsolder the crystal, X1. Install in its place the new 8.0 MHz crystal. Be sure to bend the leads so that the crystal is flat against the board.

This doubles the frequency of all clock lines on the board: CLK, CO-C15, \overline{O} , \overline{VS} , \overline{HS} , TxCLK. Since the microprocessor used in the CIP is a 6502A, ⁱⁿ which is rated to run at 2.0 MHz, this modification will also double the speed of your computer. The author has some reservations about running the CIP at 2 MHz, as this speed may be pushing the system RAMs (550ns) at their limit. The author's system has been running at this speed for over 150 hours with no apparent read or write errors, but in anticipation of individual variations in different CIP's a modification to return the speed to 1 MHz will be given.

NOTE: It seems that OSI has recently been using cheaper parts in the CIP. If your computer is new chances are that it will not run at 2 MHz. This will in no way affect the video modifications.

MEMORY, SYNC, ETC.

The CIP uses multiplexer circuitry so that the video address lines may be connected either to the video circuitry or the system address buss. Normally, the video display memory is connected to the video circuitry. However, when the system address buss specifies an address between D000 and D3FF (hex), the multiplexer switches connection of the video address lines (VA0 - VA9) to the address buss.

Control of the video RAM is directed by lines: \overline{WVE} , \overline{RVE} , \overline{MCS} , \overline{VA} . Since the video RAM will be expanded to occupy addresses D000 - D7FF (hex) the address decoding for the above mentioned signals must be altered accordingly.

Refer to FIG 1:

- 1) Cut the ($\overline{A10}$) trace to U20 pin 1.
- 2) Connect U20 pin 1 to the adjacent Vcc buss.
- 3) Cut the (\overline{WKB}) trace to U20 pin 11.
- 4) Connect the previously cut (\overline{WKB}) trace to U20 pin 10.
- 5) Cut the (\overline{RKB}) trace at the point shown, where it runs next to the GND buss.
- 6) Connect the previously cut (\overline{RKB}) trace to U20 pin 14.

Be sure that all cut traces are cut all the way through. An easy way to do this is to make two parallel cuts across the trace approximately 1/16th of an inch apart. Then, with the point of your blade, scrape off the small piece between the cuts.

Also, try to keep your wires as short and direct as possible.

Refer to FIG 2:

- 7) Cut the ($\overline{A10}$) trace on the component side of the board at the plated through hole, where it emerges just under the rightmost prototyping area (U26).

Not shown:

- 8) Connect U56 pin 1 and U56 pin 2 together on the foil side of the board.
- 8.5) Cut the (C15) trace from U65 pin 1 where it runs on the foil side of the board, near the thru-hole as in FIG 7.

Refer to FIG 3:

- 9) Cut the (C7) trace from U59 pin 11 at the plated through hole on the component side of the board as shown just above and to the left of U59.

- 10) Cut the (C11) trace from U54 pin 6 at the plated through hole just above U54, as shown.

Refer to FIG 4:

- 11) Cut the (GND) trace to U55 pin 10 on the foil side of the board.
- 12) Cut the ($\overline{02}$) trace where it runs next to the GND buss just above U41, the character generator ROM.
- 13) Solder two 16 pin DIP sockets in the two rightmost prototyping areas (U26, U27).
- 14) Connect U26 pin 8 to the GND buss. Connect U26 pin 16 to the Vcc buss.
- 15) Connect U27 pin 8 to the GND buss. Connect U27 pin 1 to the Vcc buss.
- 16) Using short pieces of wire, connect U26 pins 3, 8, 14, and 15 together.
- 17) Using short pieces of wire, connect U27 pins 3, 4, 5, 6, and 8 together.
- 18) Connect the previously cut ($\overline{02}$) trace to U26 pin 1, as shown.
- 19) Connect U55 pin 10 to U26 pin 12.
- 20) Connect U55 pin 11 to U26 pin 5.
- 21) Connect U55 pin 13 to U26 pin 10.
- 22) Connect U55 pin 14 to U26 pin 4.
- 23) Connect U26 pin 2 to the ($\overline{A10}$) trace which runs directly below the Vcc buss under U26, as shown.
- 24) Connect U26 pin 13 to U27 pin 14.
- 25) Connect U27 pins 9 and 16 together and to the Vcc buss directly under U27.
- 26) Connect U27 pin 10 to U 61 pin 15.
- 27) Connect U27 pin 2 to U30 pin 2.
- 28) Connect U27 pin 14 to U65 pin 1.
- 29) Connect U27 pin 7 to U30 pin 15.
- 30) Connect U60 pin 14 to U54 pin 6.
- 31) Connect U60 pin 14 to the trace which runs directly below the topmost Vcc buss on the board, as shown.
- 32) Connect U41 pin 6 to the (C11) trace which runs between the two related through holes above U54, as shown.
- 33) Cut the (C4) trace which runs just above the GND buss over U54, as shown.
- 34) Connect the previously cut (C4) trace to U59 pin 13.

Refer to FIG 5:

- 35) Cut the three (C10), (C9), (C8) traces to U41 pins 6, 7, and 8.
- 36) Connect the middle (C9) trace to U41 pin 8.
- 37) Connect the right (C10) trace to U41 pin 7. Leave the left (C8) trace unconnected.

Refer to FIG 6:

- 38) Making very sure to correctly orient them in the same direction, piggyback two of the new 2114L memory chips as shown. Be absolutely certain that all pins of the top chip are in contact with the corresponding pins on the lower chip, except pin 8. Bend pin 8 of the upper chip away from pin 8 of the lower chip.

Carefully, using a low wattage iron, solder all corresponding pins of the upper & lower chips together (except, as noted above, pins 8).

Solder a 6" length of ww wire to pin 8 of the upper chip as shown.

- 39) Repeat step (38) for the remaining two new 2114L's.
- 40) Making sure they are oriented correctly, insert the two piggy-backed 2114L assemblies into sockets U39 and U40.
- 41) Route the two wires from pin 8 through the nearest plated through holes to the foil side of the board and connect them to U55 pin 12.
- 42) Insert the 74LS139 into socket U26. Be sure orientation is correct.
- 43) Insert the 74LS163 into socket U27. Be sure orientation is correct.

This completes the hardware modifications to your CIP. Recheck all connections to insure they are correct. Make especially sure that pin 8 of the upper and lower 2114L's do not touch.

Reinstall the circuitboard and reconnect the power and interface connectors. Turn on the television and then the CIP. The screen should fill with random characters. Some adjustment of Horiz, Vert, Bright, and Cont may be necessary to obtain the best picture.

If the screen remains dark or if standard characters are not seen, remove power immediately and recheck all wiring.

Best picture quality and the most characters per line are obtained by direct connection of the CIP video signal to your television's video amplifier stage. This bypasses the sound trap and some of the lower bandwidth sections of the television. This modification is described in many computer magazines and will not be covered here. Also, try decreasing the low voltage control of your set as this may allow you to fit more characters per line.

Software:

The subroutine which runs the video display on the CIP is located in BASIC ROM 4, at address BF2D (hex). Since OSI uses this ROM in several of their computers, the subroutine relies on parameters located in the monitor PROM to determine the number of characters per line. These are as follows:

<u>LOCATION</u>	<u>VALUE</u>	<u>FUNCTION</u>
FFEØ	65	Position of cursor after CR, LF.
FFE1	17	Characters per line - 1.
FFE2	ØØ	Video memory size. (ØØ = 1K, any other number = 2K).

If one has the capability to program PROMs, the most elegant way to reset the display parameters is to simply program a duplicate monitor ROM, changing as necessary the above three addresses. Most of us, however, lack this capability and must resort to a software patch. The patch given below is essentially the same as the BASIC subroutine, but since it is in RAM, the line length, cursor position etc. may be user specified. In addition, it contains a machine language screen clear function so that a ?CHR\$(1) will give a fast screen clear.

This is a fairly long patch, and storing it in RAM via the monitor is prohibitively time consuming. I would therefore recommend that you save it on tape in monitor loadable format the first time you load it and are sure all is well. A good program for saving machine code programs on tape may be found in the April, 1979 issue of MICRO magazine. When placed on tape in this format, the patch takes only 19 seconds to load.

In order for this patch to work the output vector, located at Ø21A and Ø21B (hex) must be changed from FF69 to Ø222, the start address of the patch. It should be noted that this vector is reset to FF69 every time the reset key is pressed, so a reset will necessitate reloading it with Ø222. A nice feature to minimize the amount of keyboard entry is to modify the aforementioned machine language save program to output .BD11G after the patch. This will obviate the need to reset and reload the patch start address into the output vector and will automatically cold start BASIC.

This patch is relocatable, although it will require some changes. I recommend leaving it at Ø222 as this area in RAM is not used by BASIC.

With this patch in operation, the video display will consist of 30 lines (2 are lost off the top edge of the screen) by 50 to 52 characters (12 to 14 are lost in overscan).

PATCH:

Ø222	8D	Ø2	Ø2	STA	Ø2Ø2
Ø225	48			PHA	
Ø226	8A			TXA	
Ø227	48			PHA	
Ø228	98			TYA	
Ø229	48			PHA	
Ø22A	AD	Ø2	Ø2	LDA	Ø2Ø2
Ø22D	FØ	4C		BEQ	4C
Ø22F	AC	Ø6	Ø2	LDY	Ø2Ø6
Ø232	FØ	Ø8		BEQ	Ø8
Ø234	A2	4Ø		LDX	4Ø
Ø236	CA			DEX	
Ø237	DØ	FD		BNE	FD
Ø239	88			DEY	
Ø23A	DØ	F8		BNE	F8
Ø23C	C9	ØA		CMP	ØA
Ø23E	FØ	46		BEQ	46
Ø24Ø	C9	Ø1		CMP	Ø1
Ø242	DØ	1A		BNE	1A
Ø244	A9	2Ø		LDA	2Ø
Ø246	AØ	Ø8		LDY	Ø8
Ø248	A2	ØØ		LDX	ØØ
Ø24A	9D	ØØ	DØ	STAX	DØØØ
Ø24D	E8			INX	
Ø24E	DØ	FA		BNE	FA
Ø25Ø	EE	4C	Ø2	INC	Ø24C
Ø253	88			DEY	
Ø254	DØ	F4		BNE	F4
Ø256	A9	DØ		LDA	DØ
Ø258	8D	4C	Ø2	STA	Ø24C
Ø25B	4C	7B	Ø2	JMP	Ø27B
Ø25E	C9	ØD		CMP	ØD
Ø26Ø	DØ	Ø6		BNE	Ø6
Ø262	2Ø	D2	Ø2	JSR	Ø2D2
Ø265	4C	7B	Ø2	JMP	Ø27B
Ø268	8D	Ø1	Ø2	STA	Ø2Ø1
Ø26B	2Ø	C8	Ø2	JSR	Ø2C8
Ø26E	EE	ØØ	Ø2	INC	Ø2ØØ
Ø271	A9	F9		LDA	F9*
Ø273	CD	ØØ	Ø2	CMP	Ø2ØØ
Ø276	3Ø	ØB		BMI	ØB
Ø278	2Ø	DA	Ø2	JSR	Ø2DA
Ø27B	68			PLA	
Ø27C	A8			TAY	
Ø27D	68			PLA	
Ø27E	AA			TAX	
Ø27F	68			PLA	
Ø28Ø	4C	6C	FF	JMP	FF6C

Linefeed?

Screen clear?

Screen clear subroutine.

Carriage Return?

Ø283	2Ø D5 Ø2	JSR Ø2D5
Ø286	2Ø C8 Ø2	JSR Ø2C8
Ø289	A9 BF	LDA BF+
Ø28B	EA	NOP
Ø28C	EA	NOP
Ø28D	8D Ø2 Ø2	STA Ø2Ø2
Ø29Ø	A2 Ø7	LDX Ø7
Ø292	BD F3 BF	LDAX BFF3
Ø295	9D Ø7 Ø2	STAX Ø2Ø7
Ø298	CA	DEX
Ø299	1Ø F7	BPL F7
Ø29B	A2 D7	LDX D7
Ø29D	A9 4Ø	LDA 4Ø
Ø29F	8D Ø8 Ø2	STA Ø2Ø8
Ø2A2	AØ ØØ	LDY ØØ
Ø2A4	2Ø Ø7 Ø2	JSR Ø2Ø7
Ø2A7	DØ FB	BNE FB
Ø2A9	EE Ø9 Ø2	INC Ø2Ø9
Ø2AC	EE ØC Ø2	INC Ø2ØC
Ø2AF	EC Ø9 Ø2	CPX Ø2Ø9
Ø2B2	DØ FØ	BNE FØ
Ø2B4	2Ø Ø7 Ø2	JSR Ø2Ø7
Ø2B7	CC Ø2 Ø2	CPY Ø2Ø2
Ø2BA	DØ F8	BNE F8
Ø2BC	A9 2Ø	LDA 2Ø
Ø2BE	2Ø ØA Ø2	JSR Ø2ØA
Ø2C1	CE Ø8 Ø2	DEC Ø2Ø8
Ø2C4	DØ F8	BNE F8
Ø2C6	FØ AE	BEQ AE
Ø2C8	AE ØØ Ø2	LDX Ø2ØØ
Ø2CB	AD Ø1 Ø2	LDA Ø2Ø1
Ø2CE	9D ØØ D7	STAX D7ØØ
Ø2D1	6Ø	RTS
Ø2D2	2Ø C8 Ø2	JSR Ø2C8
Ø2D5	A9 C8	LDA C8#
Ø2D7	8D ØØ Ø2	STA Ø2ØØ
Ø2DA	AE ØØ Ø2	LDX Ø2ØØ
Ø2DD	BD ØØ D7	LDAX D7ØØ
Ø2EØ	8D Ø1 Ø2	STA Ø2Ø1
Ø2E3	A9 5F	LDA 5F
Ø2E5	DØ E7	BNE E7

Output Vector: Ø21A 22 Ø2

Cold Start: .BD11 G

Warm Start: .A274 G

* Cursor starting position + no of characters per line - 1.

+ Cursor starting position - no of characters lost in left overscan.

Cursor starting position.

NOTE: The above three addresses may have to be adjusted from the values given to suit your particular TV or monitor.

 
 
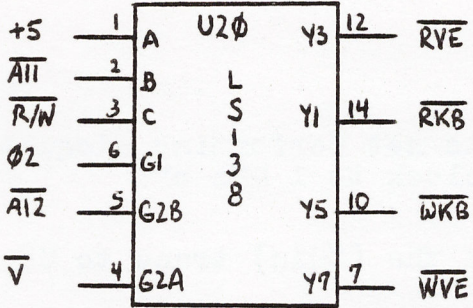


FIG 1
FOIL SIDE

 
 


FIG 2
COMPONENT
SIDE

 


FIG 3
COMPONENT
SIDE

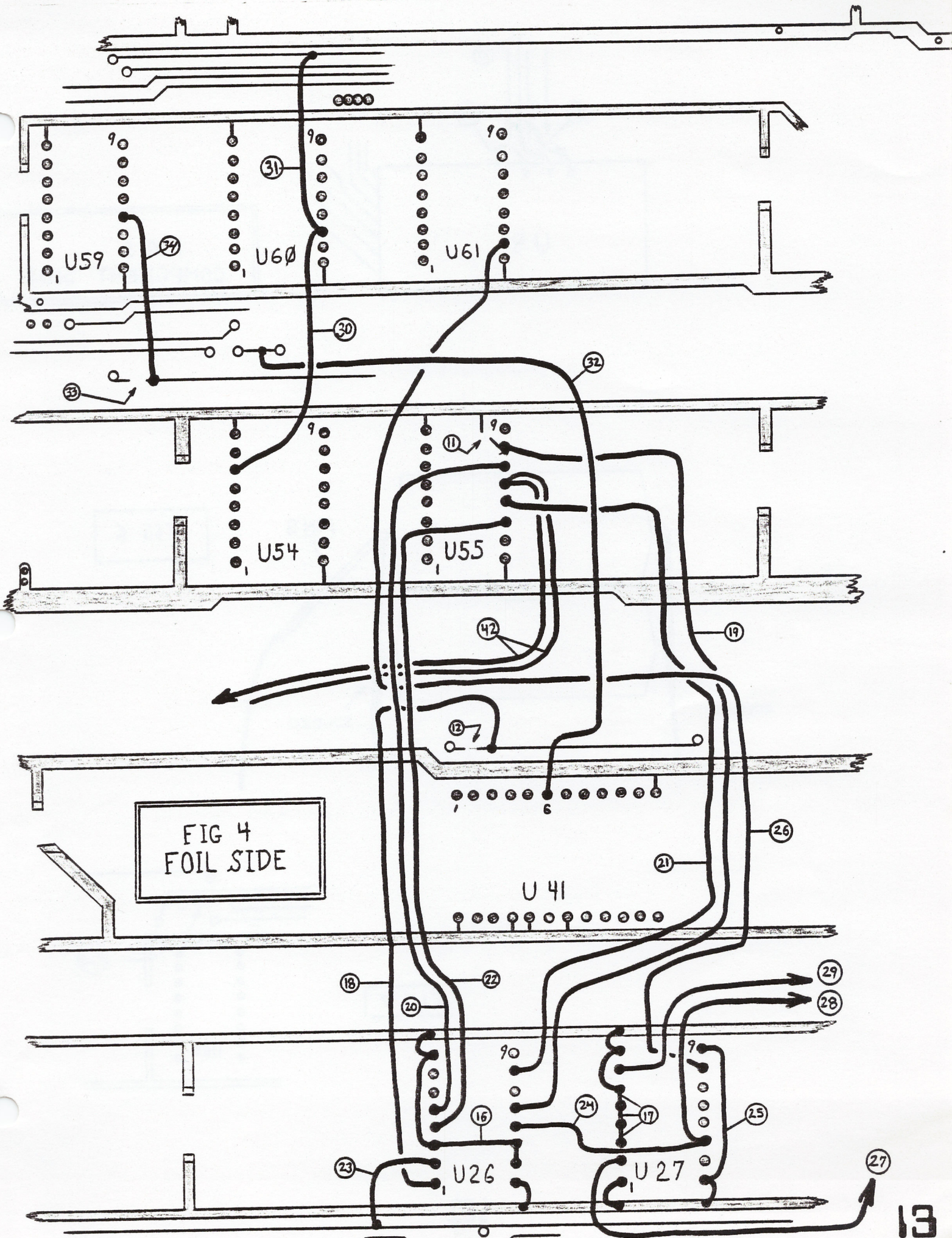


FIG 4
FOIL SIDE

 


FIG 5
COMPONENT SIDE

 


FIG 6

FIG 7

